

# Memory Interfacing with 8088 Microprocessor

# Fundamentals


- Address decoding
- Glue logic
- Type of memory (RAM or ROM)
- Memory map
- Labelling the schematic
- Reverse engineering the schematic  
(determining memory map, memory size and type of memory etc.)

# Interfacing Read-Only Memory


# Some facts to know


- In 8086 and 8088 CPUs, CS is FFFFH and IP is 0000H upon reset.
- So FFFF0H location must be found in ROM and should contain the first instruction
- As ROM cannot be written to, so WE pin is not available on ROM chips.

# Interfacing a single ROM chip

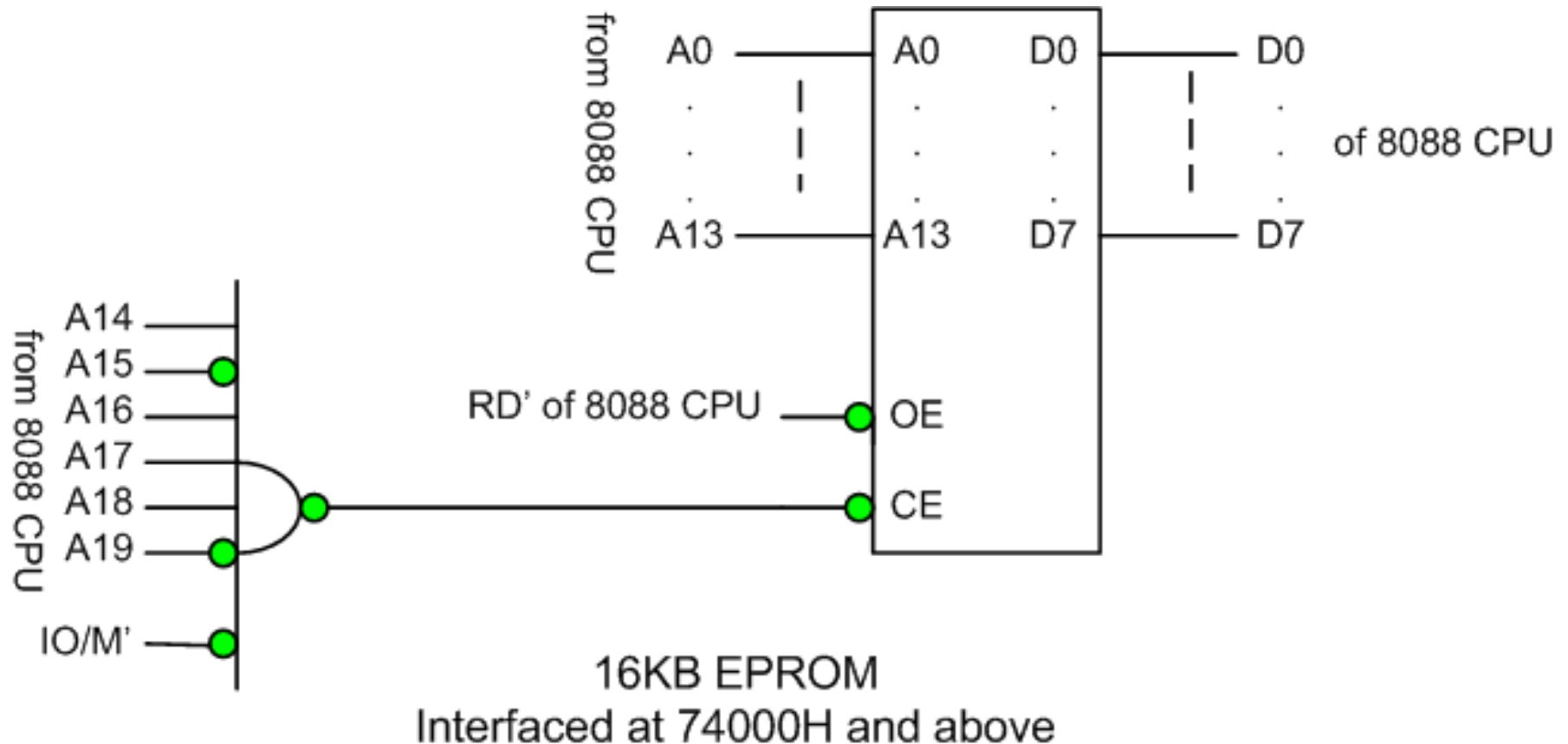

# 74LS138 3x8 Complementary Decoder

 

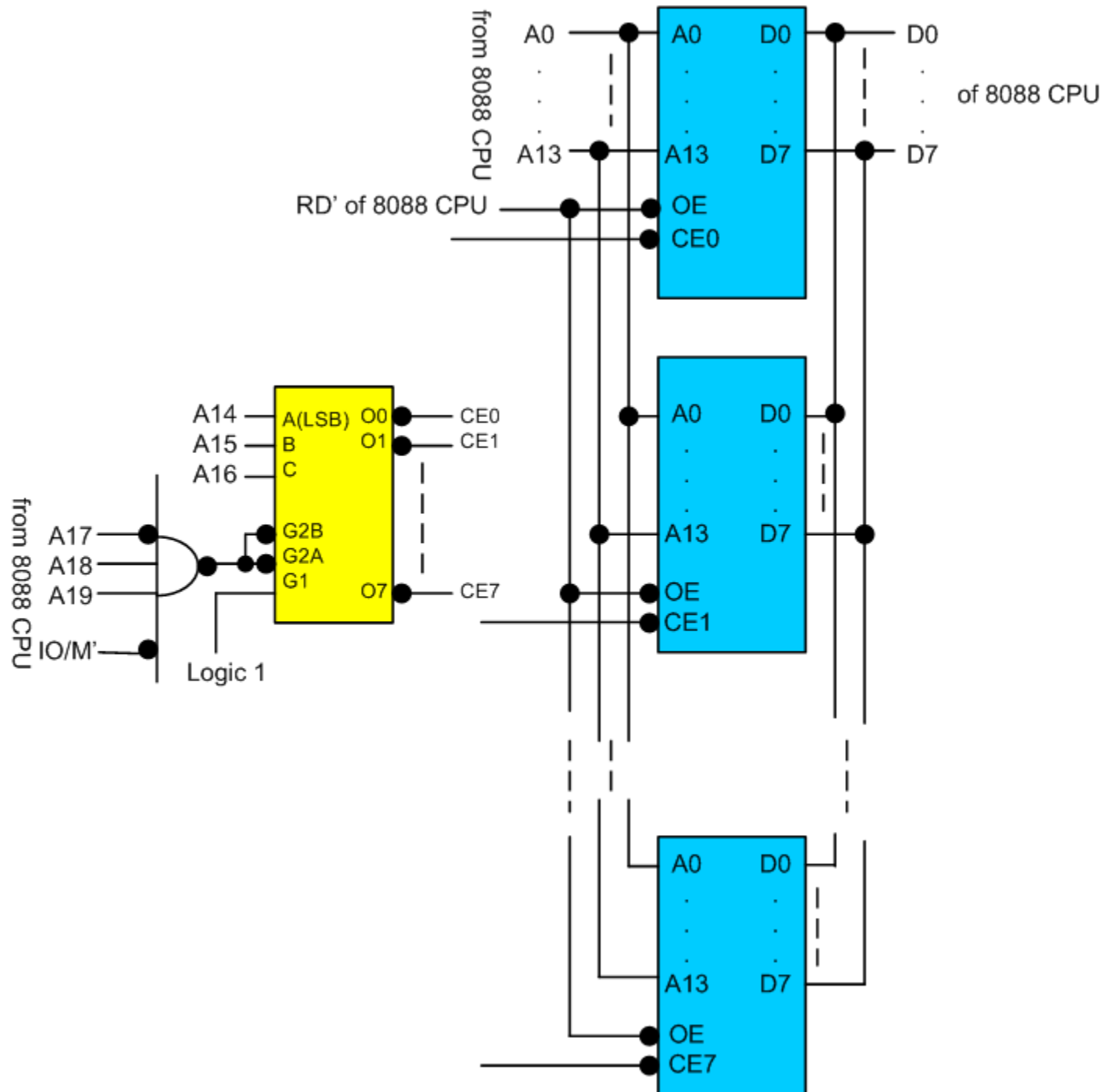


# **Interfacing Random Access Memory**



# Recall the SRAM

- Data Bus
- Address Bus
- Order of memory
- Control Bus or Control Lines  
(OE', WR', CS'(CE' or ME'))
- Power lines (Vcc and GND)
- Tri-state or Z-state or High-impedance

# Interfacing single SRAM chip

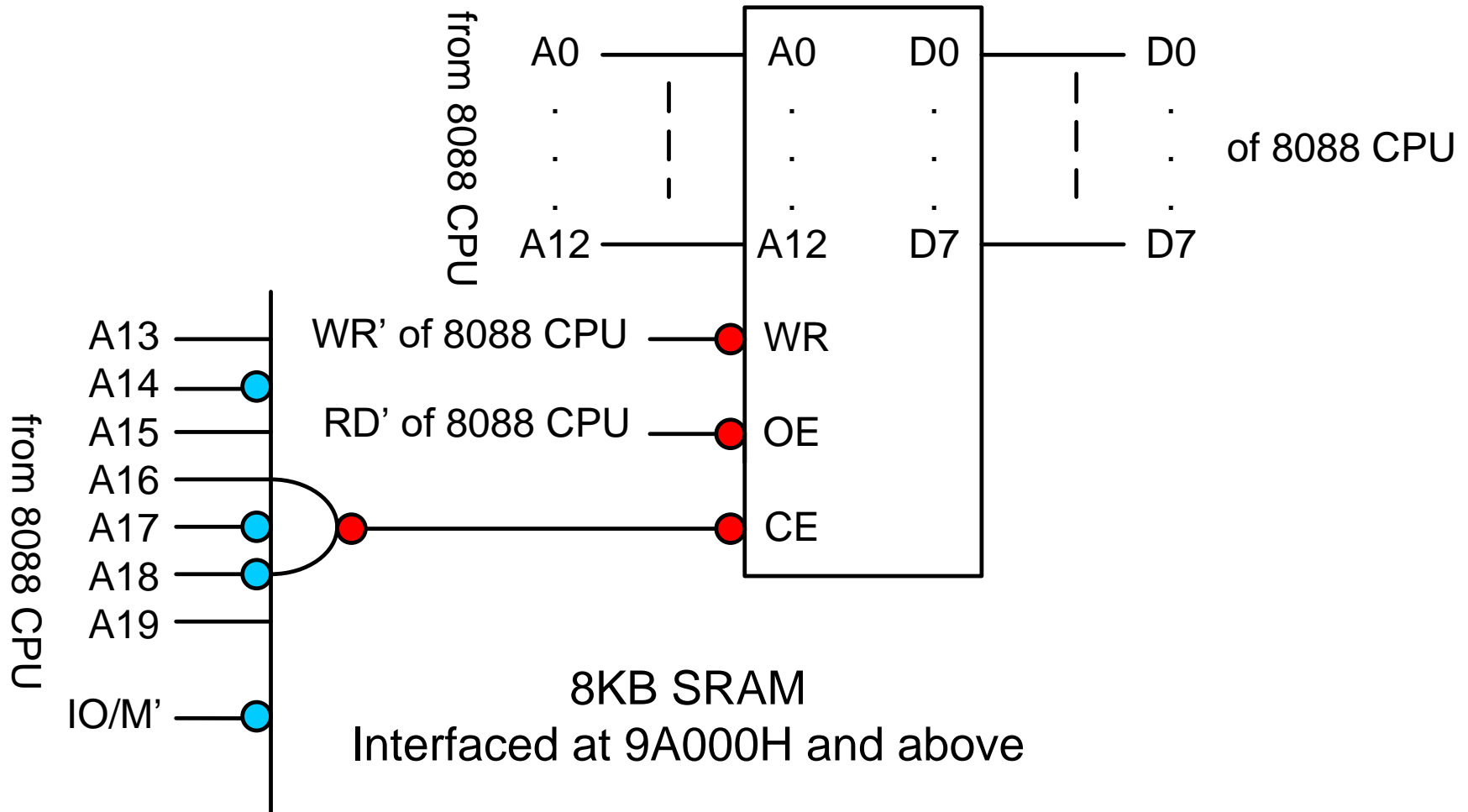

# Truth Table of 74LS138

Inputs						Outputs							
Enable			Selection										
G1	$\overline{G2A}$	$\overline{G2B}$	C	B	A	$\overline{00}$	$\overline{01}$	$\overline{02}$	$\overline{03}$	$\overline{04}$	$\overline{05}$	$\overline{06}$	$\overline{07}$
X	X	1	X	X	X	1	1	1	1	1	1	1	1
X	1	X	X	X	X	1	1	1	1	1	1	1	1
0	X	X	X	X	X	1	1	1	1	1	1	1	1
1	0	0	0	0	0	0	1	1	1	1	1	1	1
1	0	0	0	0	1	1	0	1	1	1	1	1	1
1	0	0	0	1	0	1	1	0	1	1	1	1	1
1	0	0	0	1	1	1	1	1	0	1	1	1	1
1	0	0	1	0	0	1	1	1	1	0	1	1	1
1	0	0	1	0	1	1	1	1	1	1	0	1	1
1	0	0	1	1	0	1	1	1	1	1	1	0	1
1	0	0	1	1	1	1	1	1	1	1	1	1	0

